


Buck Converter Stability checks using Richtek Fast Load Transient Tool

Richtek Field Application Engineering

December, 2016

Converter stability check methods (I)

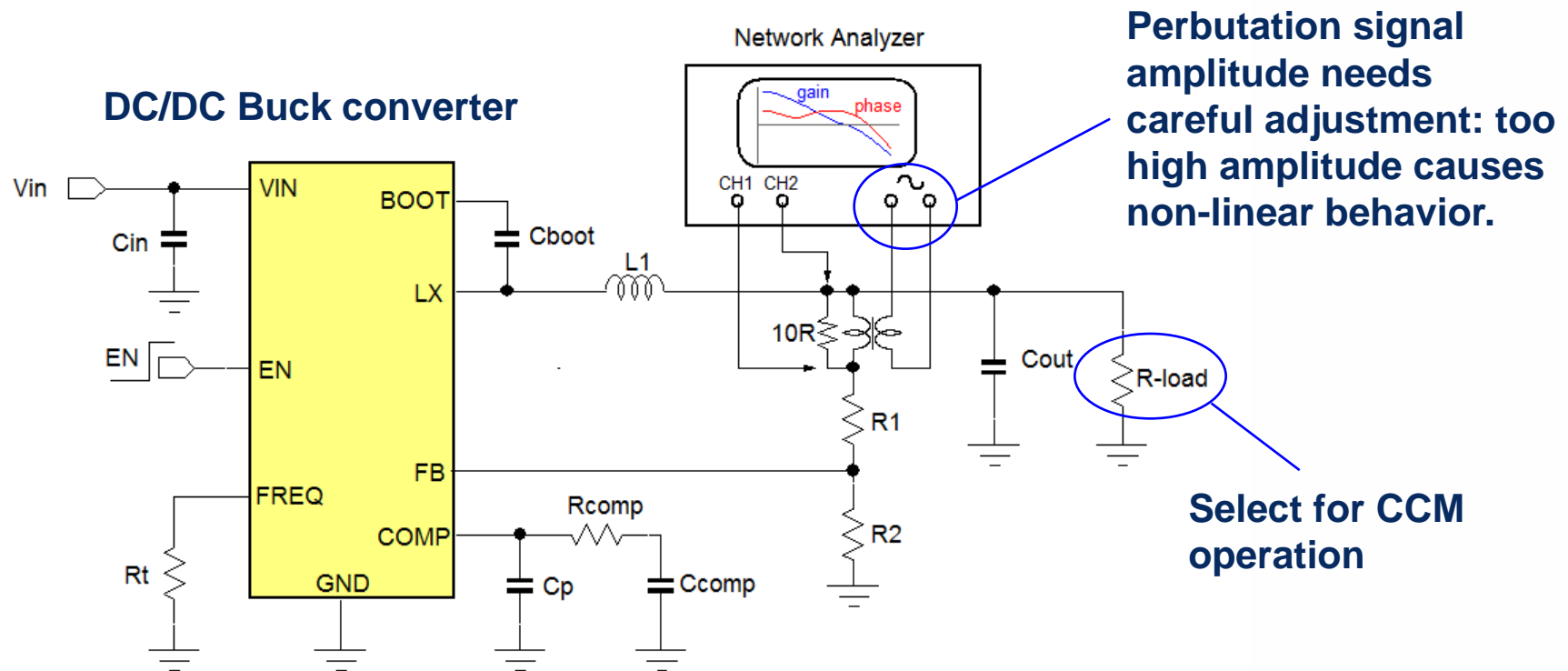Frequency Domain Open Loop Gain-Phase Analysis




- + Good overview of critical loop parameters
- Complicated measurement
- Prone to noise pick-up and non-linear effects

Converter stability check methods (II)

Time Domain Fast Load Transient Analysis



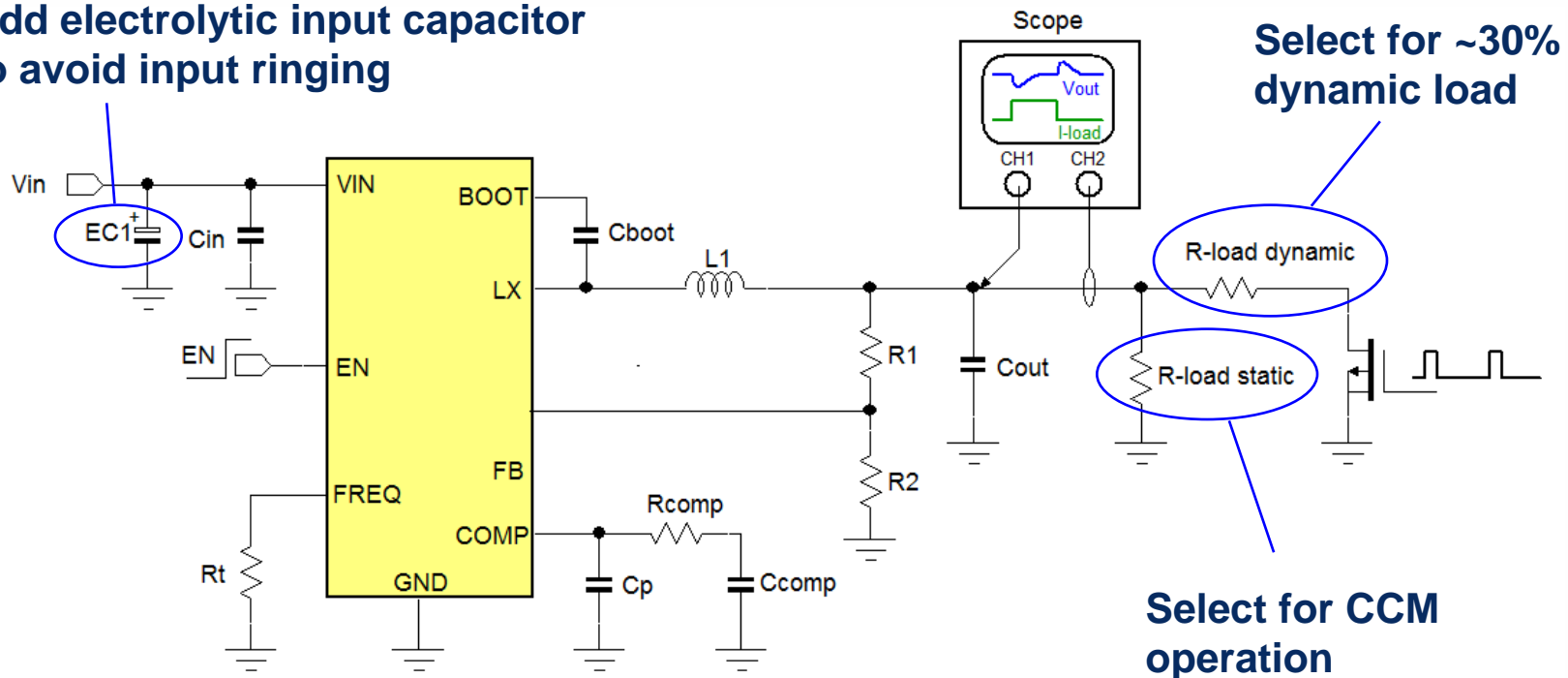
Add electrolytic input capacitor to avoid input ringing




- + Simple measurement
- + Can show various converter response effects
- Needs some skill to interpret the output waveform

Richtek Load Transient Tool measurement setup

The Load transient tool is intended to be used for testing voltage regulators (buck, boost, LDO) with output voltage between 1V and 5V and maximum 5A current rating, but basically it can be used for testing any voltage regulator output. Just apply the pulse load leads to the converter output, adjust the static load resistor for CCM (continuous current mode) or ~ 30% of rated load, select the pulse load resistor for ~ 30% of rated load, measure the pulse current and the regulator output voltage across the output capacitors. Adjust the pulse load duty-cycle / frequency to see the full step load response.

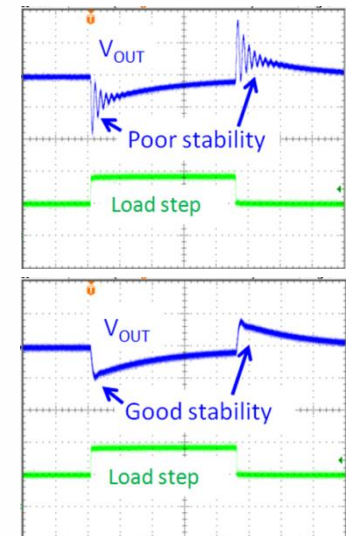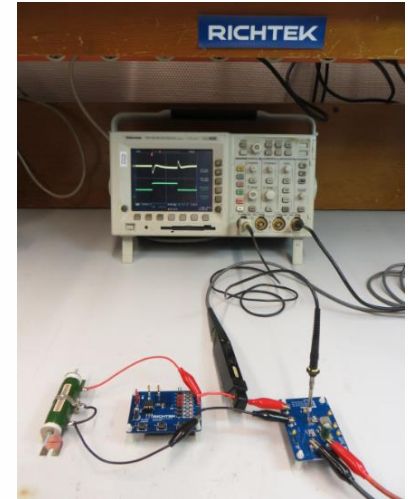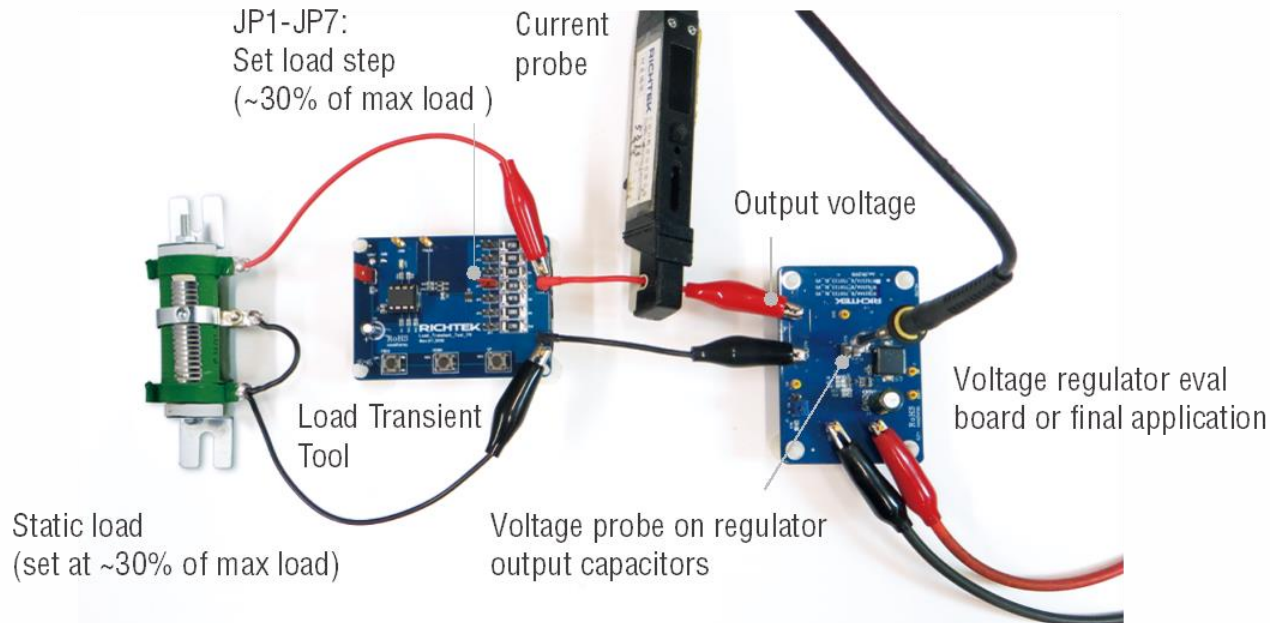

Richtek Load Transient Tool schematic

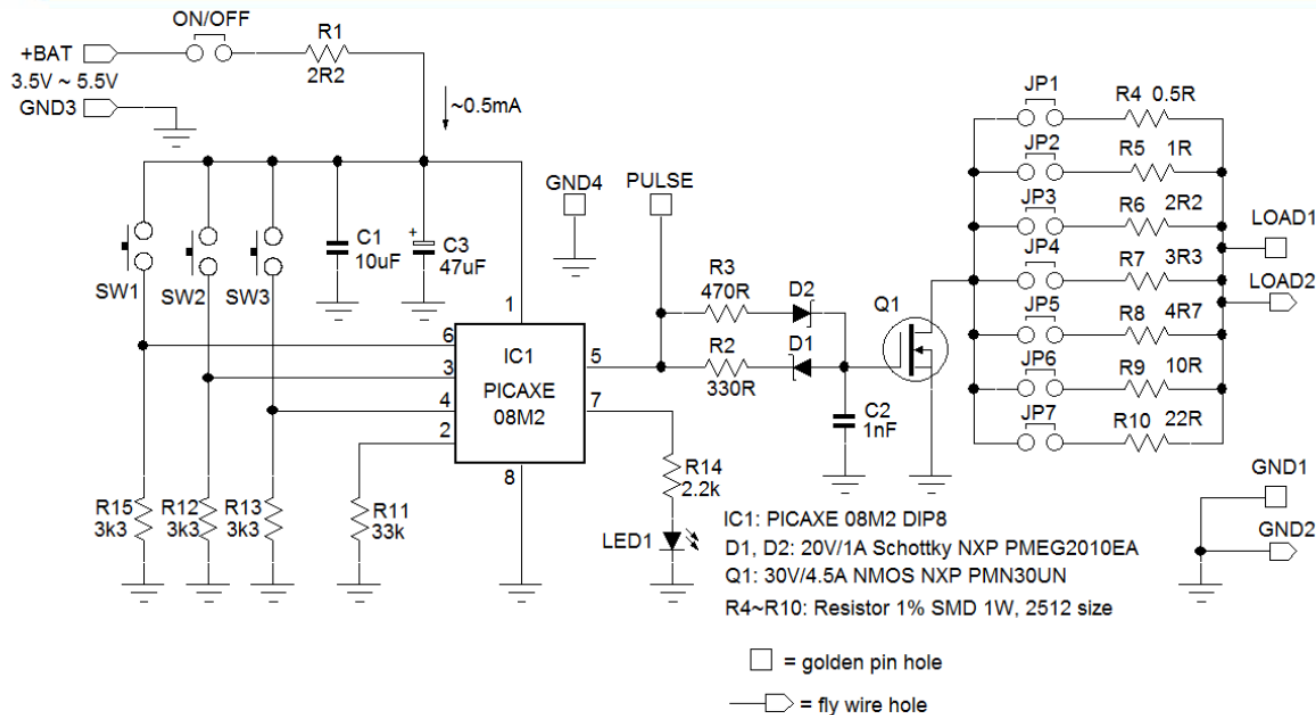




The above schematic shows the micro controller that drives the MOSFET switch. The MOSFET gate drive is designed to generate equal switching speeds with ~500nsec rise/fall times. Reducing or removing C2 can increase the switching speed, but the actual load current transient speed is mostly determined by the wiring inductance between the tool and the application. Especially when testing low voltage supplies (< 2V), it may be necessary to use short, thick wires between the tool and the application to minimize inductance.





Low inductance connection

Richtek Load Transient Tool

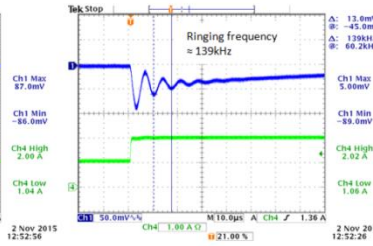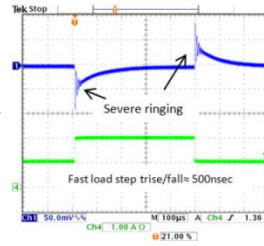
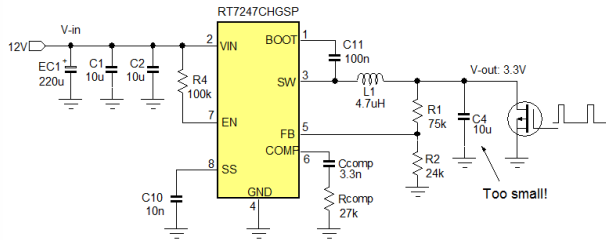
What can you do with the fast load transient tool?



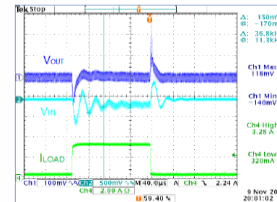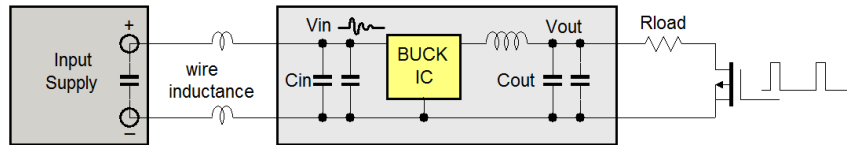**Quickly check
converter loop
stability**





**Check input
supply stability**

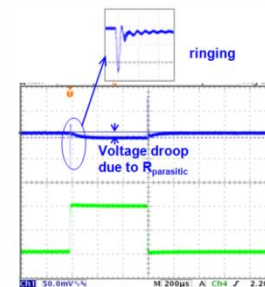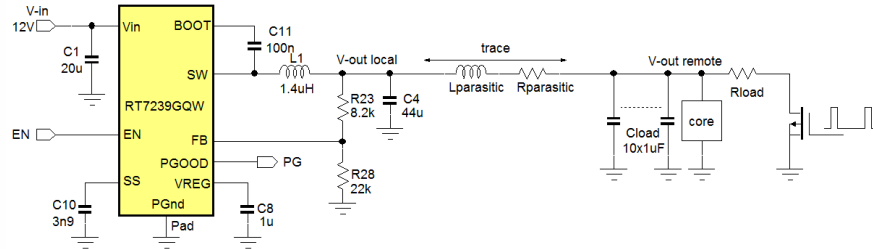

**Check layout
related problems**

....and many more: Vout sag & soar, load regulation, slope compensation issues, estimate converter bandwidth, duty-cycle limits, check LDO, Boost, Flyback

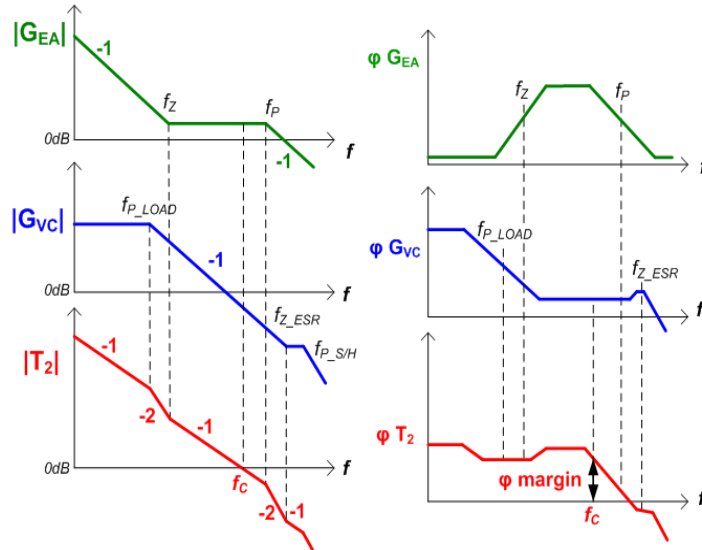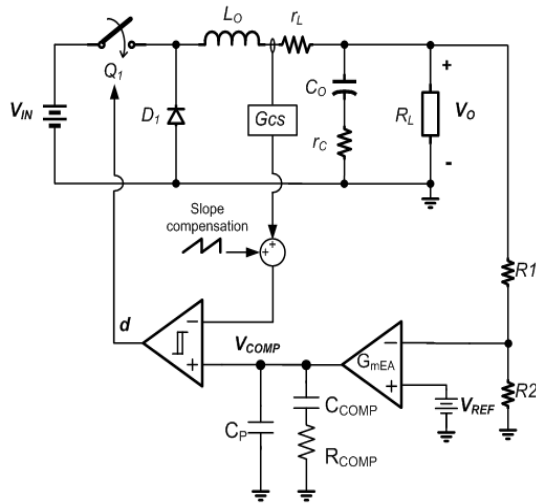Current Mode Buck converter control loop formula's



$$f_{P_LOAD} = \frac{1}{2\pi C_{OUT} \cdot R_{LOAD}}$$

$$f_{Z_ESR} = \frac{1}{2\pi C_{OUT} \cdot R_{ESR}}$$

$$f_Z = \frac{1}{2\pi C_{COMP} \cdot R_{COMP}}$$

$$f_P = \frac{1}{2\pi C_P \cdot R_{COMP}}$$

$$f_C = \frac{R_{COMP} \cdot G_{mEA} \cdot G_{CS}}{2\pi C_{OUT}} \cdot \frac{V_{REF}}{V_{OUT}}$$

Standard design values:

1. Set $F_{CONTROL}$ for $\sim 1/10$ of $F_{SWITCHING}$

$$R_{COMP} = \frac{2\pi C_{OUT} \cdot 0.1 F_{SW}}{G_{mEA} \cdot G_{CS}} \cdot \frac{V_{OUT}}{V_{REF}}$$

2. F_Z to be just below F_{P_LOAD}

$$C_{COMP} \geq \frac{C_{LOAD} \cdot R_{LOAD}}{R_{COMP}}$$


3. F_P to be close to F_{Z_ESR}

$$C_P = \frac{C_{OUT} \cdot R_{ESR}}{R_{COMP}}$$




(in noisy application with MLCC C_{out} , F_P can be set between $0.5 \sim 1 \cdot F_{SWITCHING}$)

Current Mode Buck converter

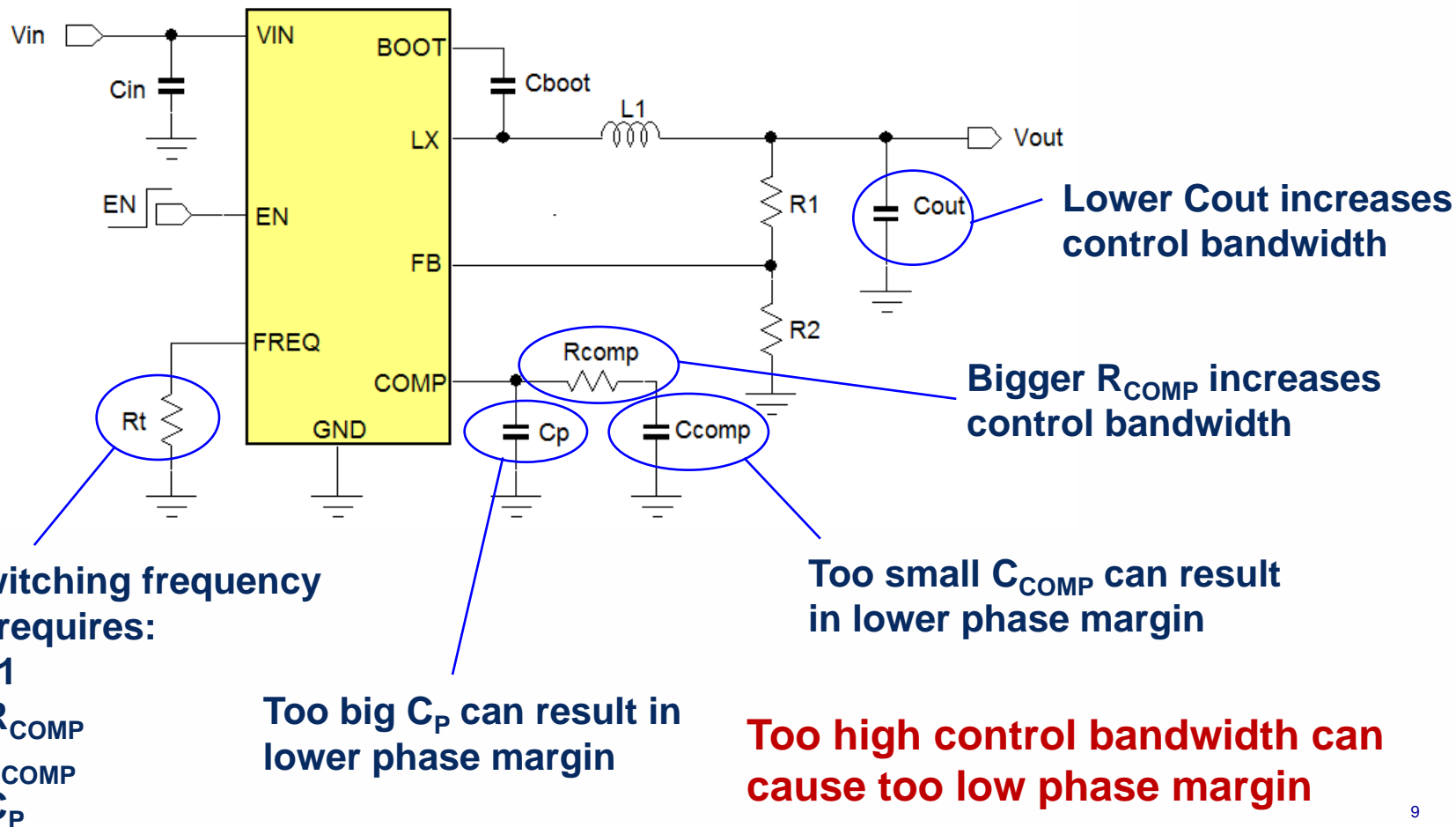
Components that influence Current Mode Buck converter loop stability



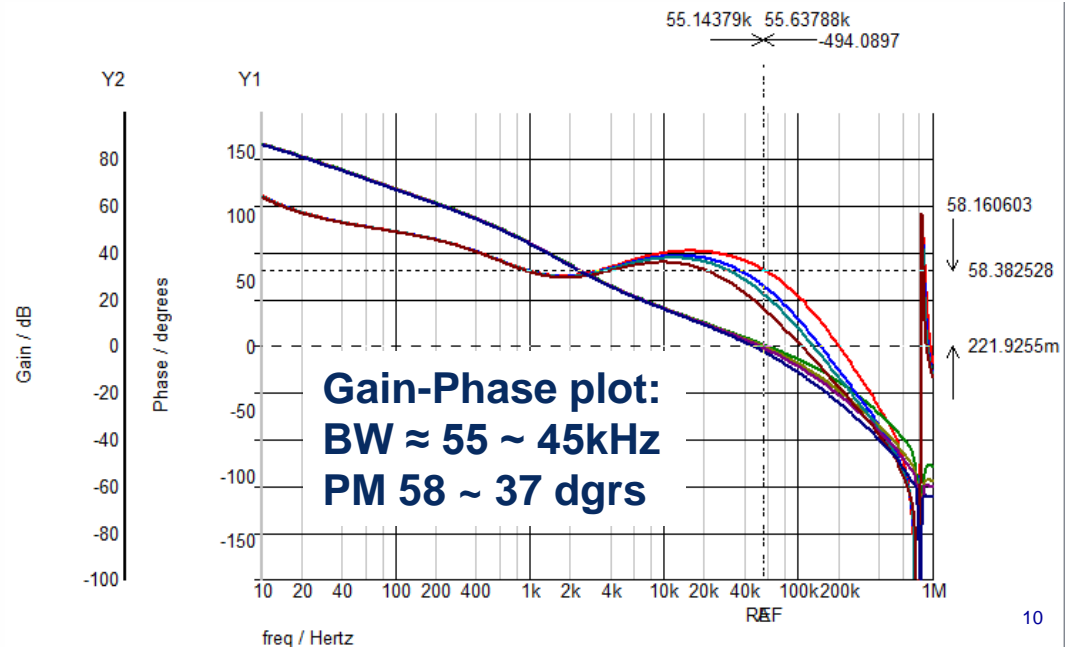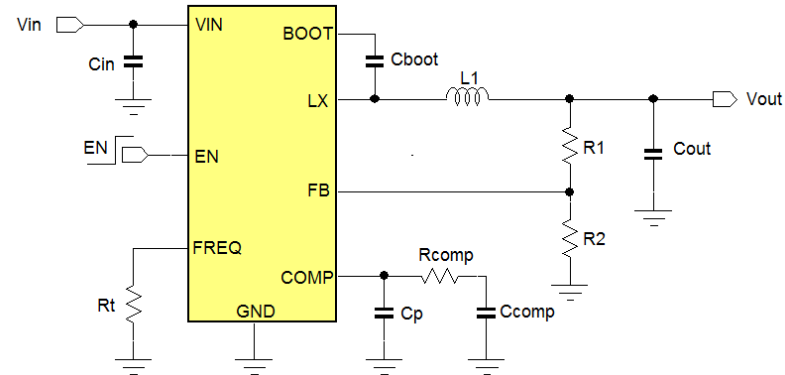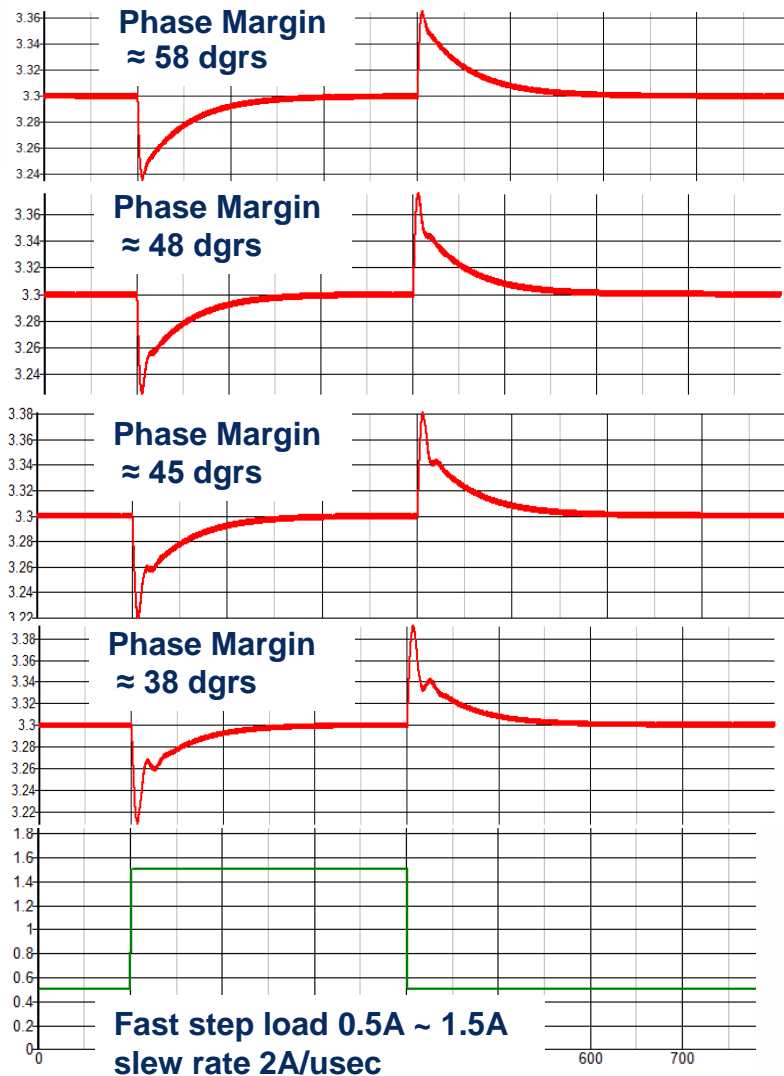Example of Fast Transient response vs. Phase Margin



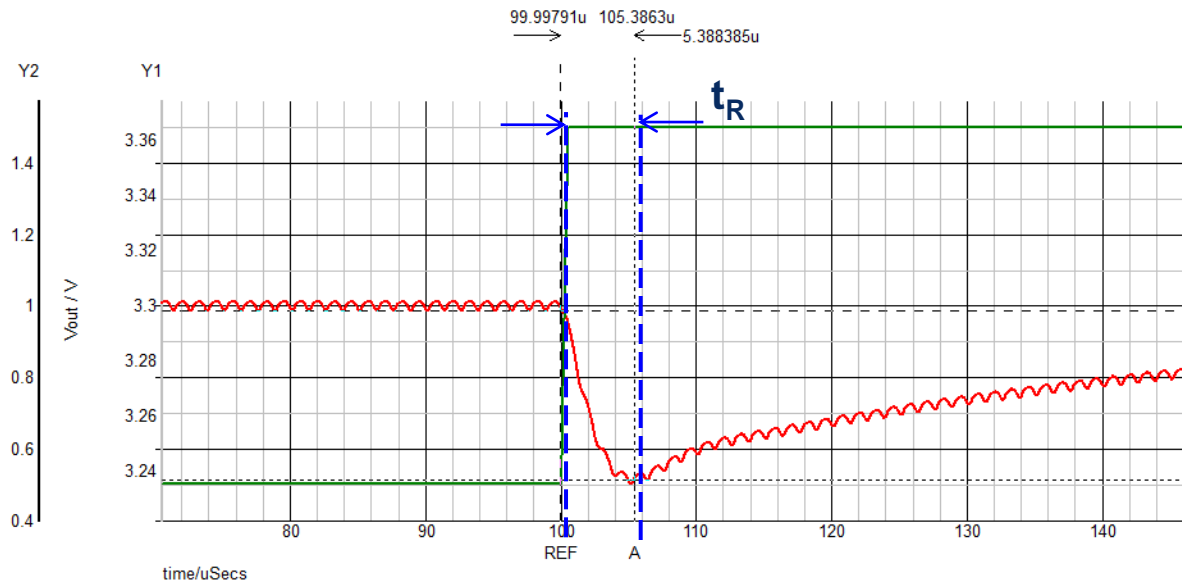What else can you learn from Fast Transient response?



Response time t_R is a rough indication of the control bandwidth:


**For most current mode buck converters:
Bandwidth $BW \approx 0.3 / t_R$**

In this example:

$t_R = 5.3\mu\text{sec}$: $\rightarrow BW \approx 0.3/5.3\mu\text{sec} = 57\text{kHz}$


**Note: Load step rise time must be \ll than $1/F_C$.
 \rightarrow Choose load step rise time around 500nsec**

Actual measurement example

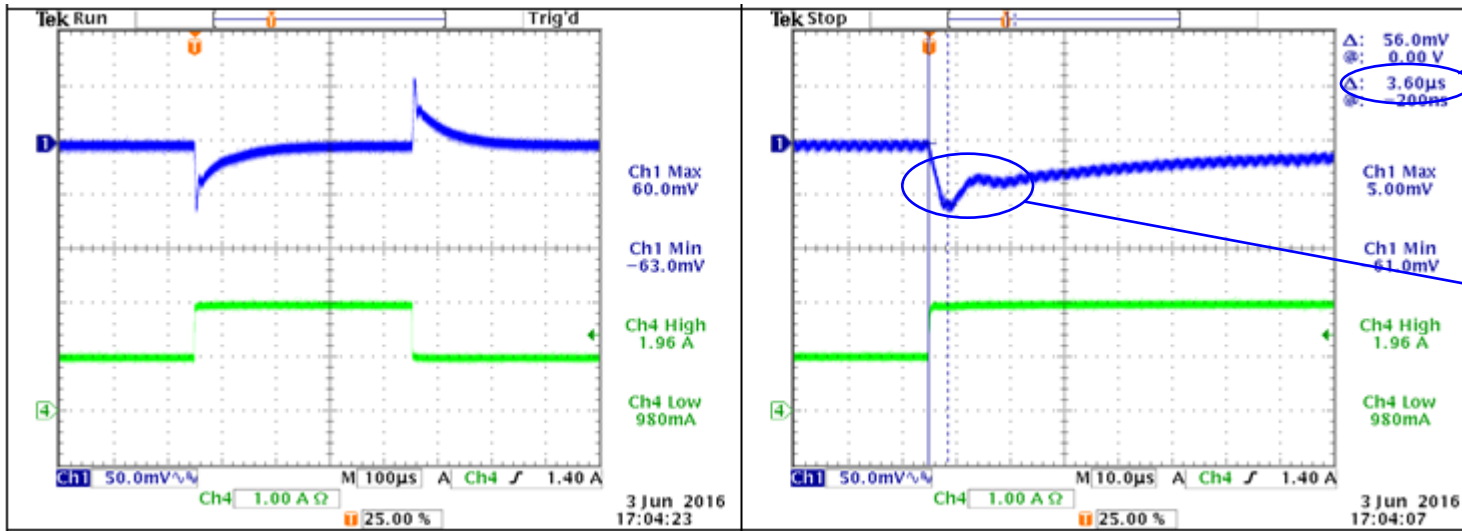

$t_R = 3.6\mu\text{sec} \rightarrow$
 $\text{BW} \approx 0.3/3.6\mu\text{sec}$
 $= 83\text{kHz}$

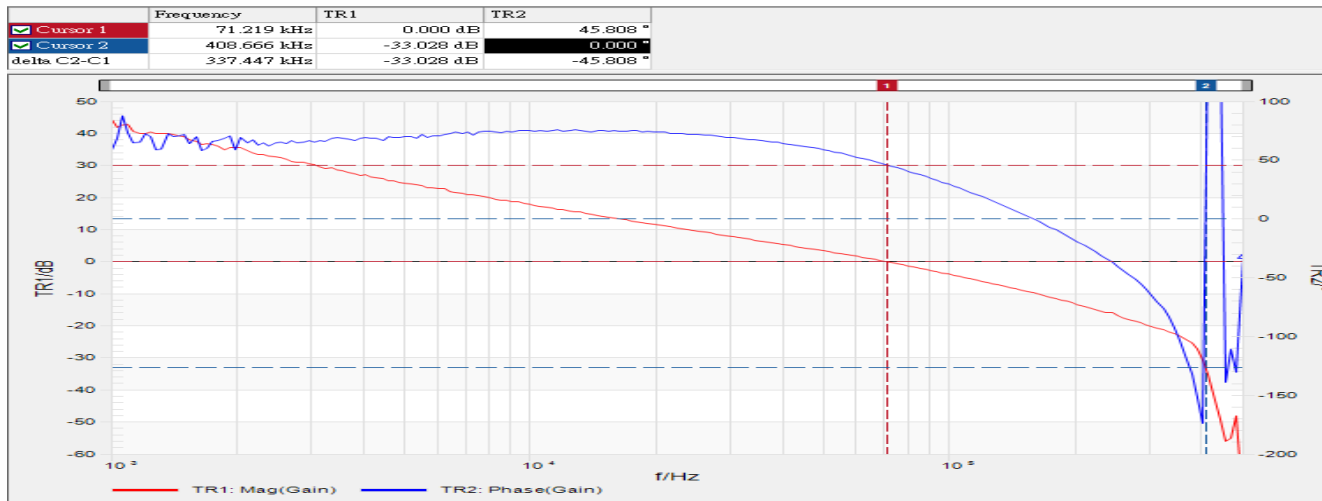Single bump: \rightarrow
 $\text{PM} \approx 45\text{ dgs}$



Actual Gain-Phase measurement:

Measured BW = 72kHz
Measured PM = 45.8 dgs

Output capacitor value is critical for loop stability!



$$f_c = \frac{R_{COMP} \cdot G_{mEA} \cdot G_{CS}}{2\pi C_{OUT}} \cdot \frac{V_{REF}}{V_{OUT}}$$

**Smaller output capacitor
increases BW!**

Source:

<http://ds.murata.com>

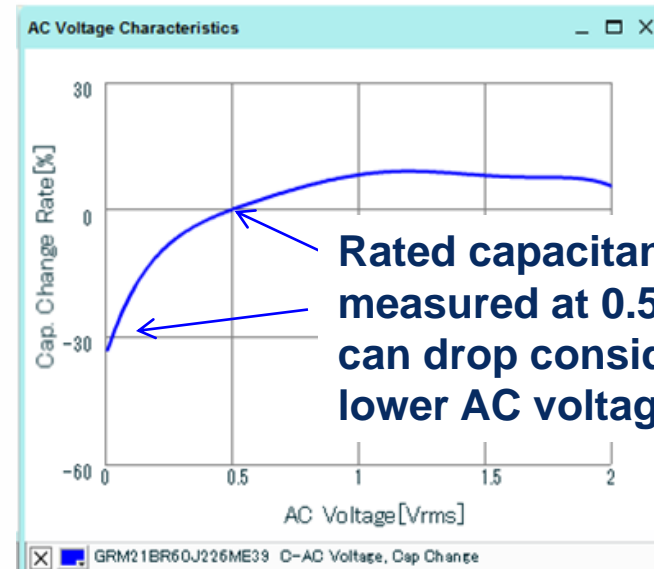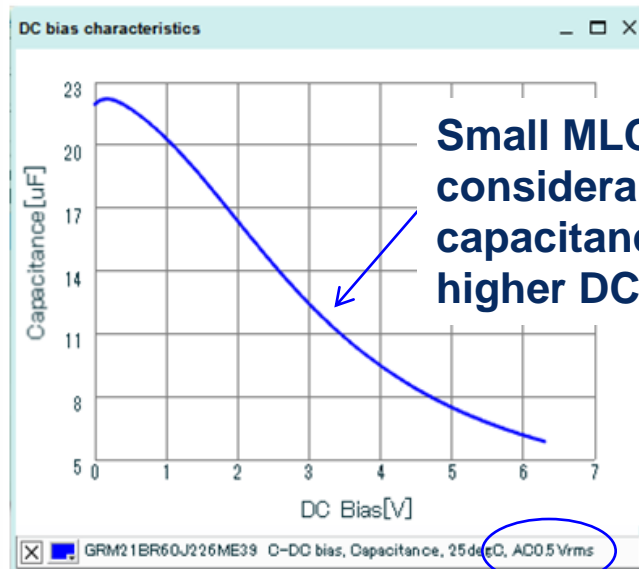
Be aware of MLCC capacitor DC bias and AC ripple characteristics: [/software/simsurfing/en-us/](http://software.simsurfing/en-us/)



(if DC bias or AC voltage effect is not specified for your capacitor type, ask for it)

→ Always use actual capacitance when designing the control loop!

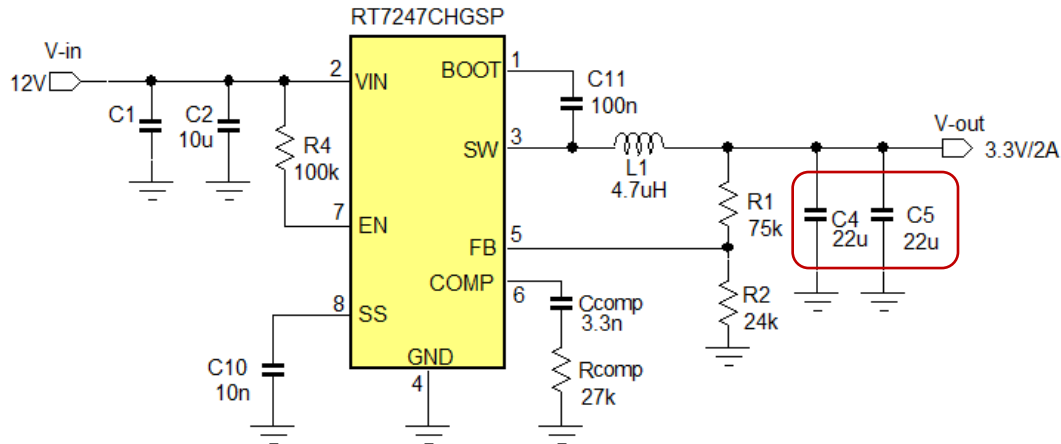
Practical example on output capacitor influence (I)



800kHz converter designed for 2x22uF output capacitance in 3.3V output application.


Circuit was designed for BW = 69kHz and PM = 59dgs

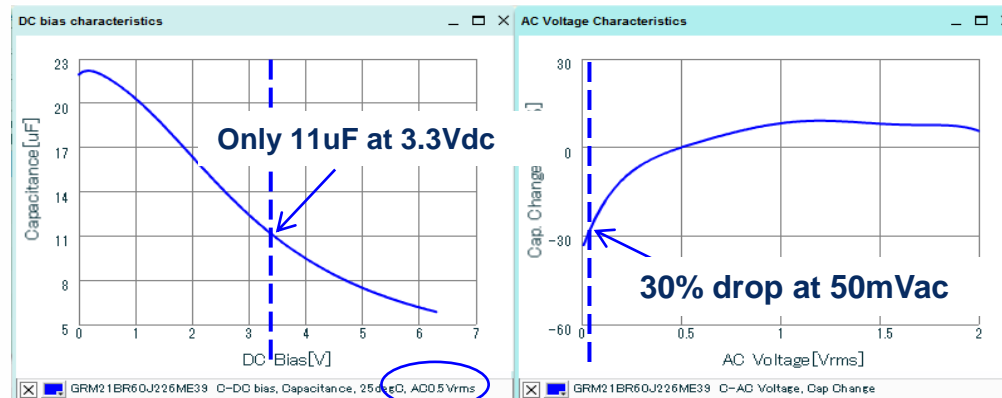Designer selects 2x 22μF / 6.3V 0805 MLCC: GRM21BR60J226ME39L




Actual capacitance is $11\mu\text{F} \times 0.7 = 8\mu\text{F}$: total output capacitance **16uF instead of 44uF**
Converter Bandwidth will become $44/16 = 2.75$ times higher than design value.

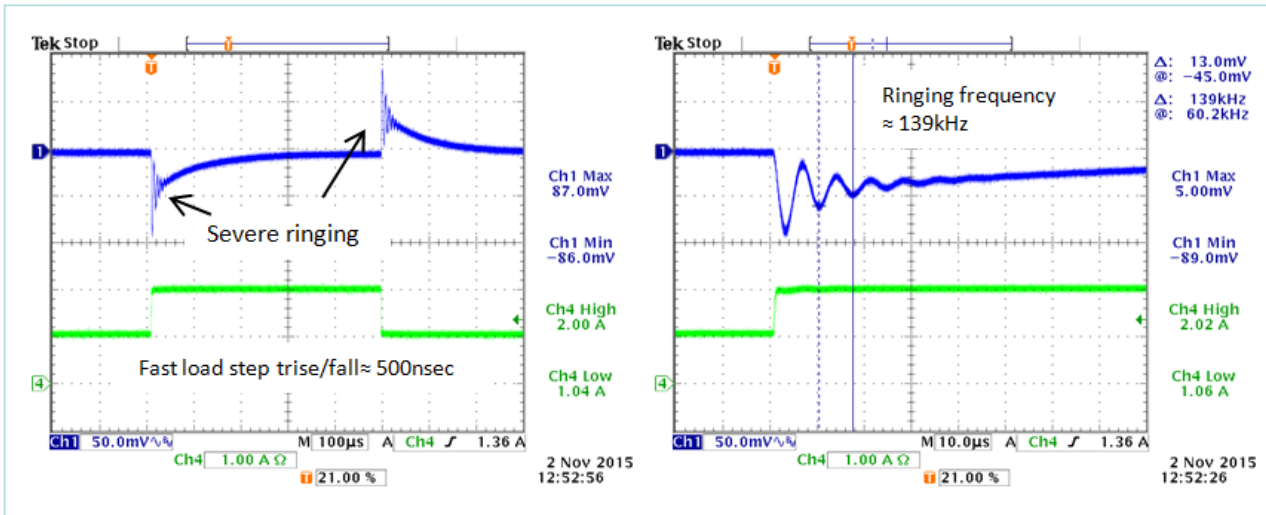Practical example on output capacitor influence (II)



Step load shows severe ringing with ringing frequency of 139kHz

(Ringing frequency indicates F_c value)

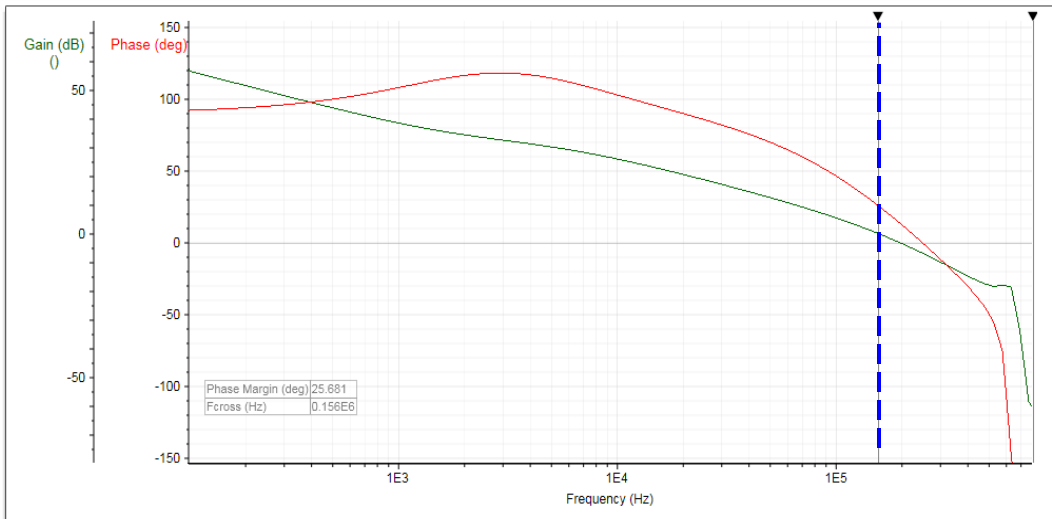

Circuit simulation using online Richtek Designer tool and using 16uF output capacitance confirms the step load result:


BW = 156kHz and PM = 26dgs

→ You can reduce R_{COMP} to reduce the BW to original design value for better PM.


ACOT™ Buck converter stability

ACOT buck converters are much less critical in stability compared to current mode buck converters.

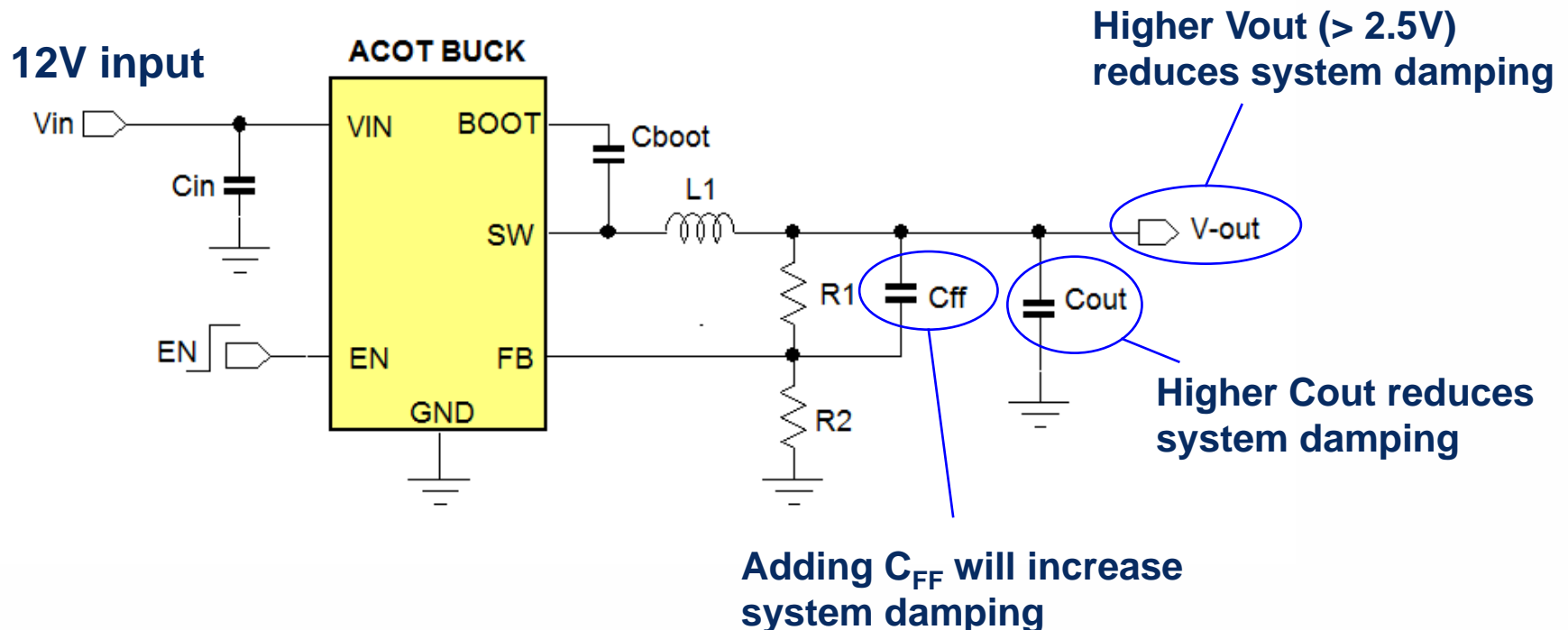Normally applications with higher duty-cycle (> 20%) or large value output capacitors need to add some C_{FF} to increase system damping.




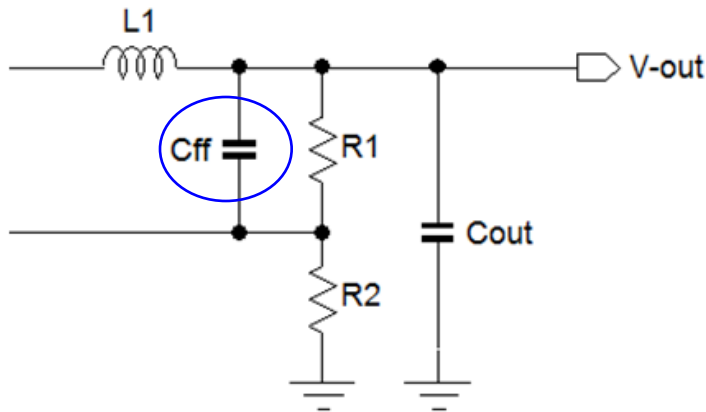ACOT converter stability: How to tune Cff



The feed-forward capacitor plays a role in the damping of the ACOT control loop, especially at higher duty-cycle applications like 12V → 5V. For low duty-cycle applications like 12V → 1V it is normally not needed. The value of Cff for a specific ACOT converter depends on duty-cycle, C_{OUT} value, inductor value and R1 value.

Practical method to find Cff value:

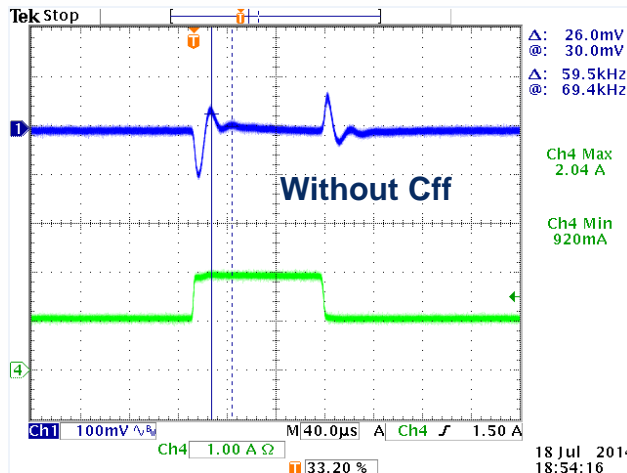


2. Calculate Cff by the formula:

$$C_{FF} = \frac{1}{2\pi \cdot R1 \cdot f_{RING} \cdot 0.8}$$

In this example: (R1 = 120k)

$$\frac{1}{2\pi \cdot 120k \cdot 59.5k \cdot 0.8} = 27.9pF$$

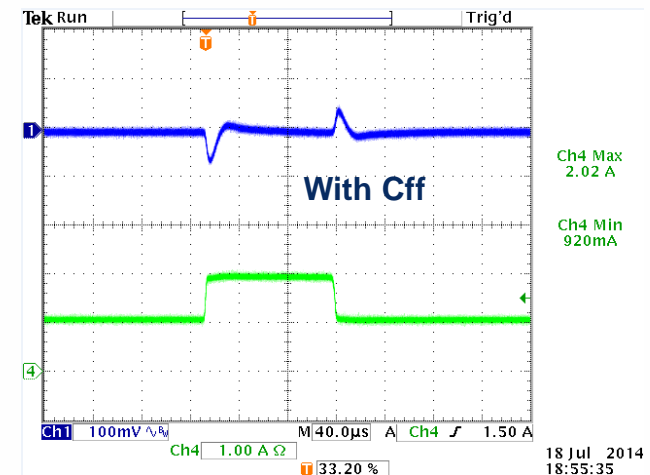1. Apply a fast step load and if it shows ringing, measure the ringing frequency
In this 12V → 5V example: $f_{RING}=59.5kHz$



After adding Cff = 27pF: well-damped step response

Relevant Richtek application note

AN038: Fast Load Transient Testing

Richtek Application AN038

Let's show this with the below example where a RT7294CGJ6F, a low cost 18V/2.5A ACOT buck IC in SOT-23-6 is used to make a 1V core supply rail:

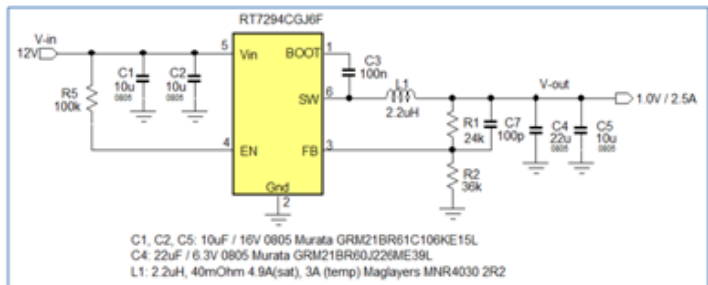


FIGURE 41

Technical explanation



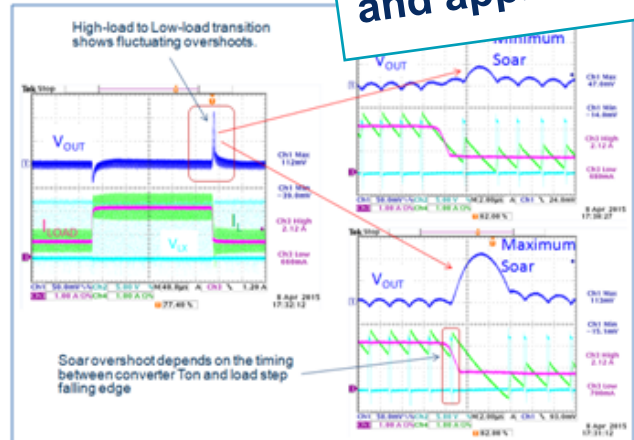
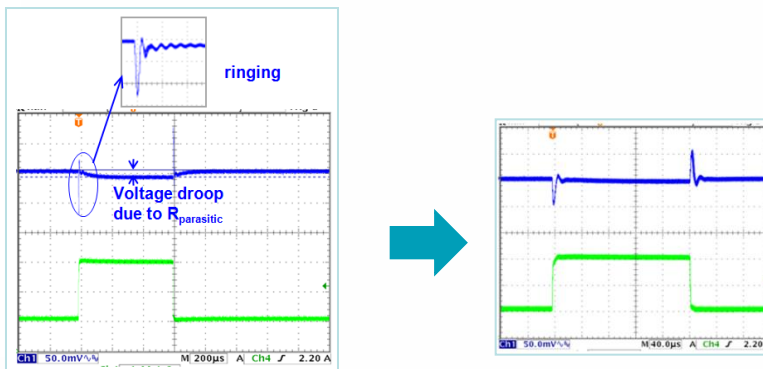


FIGURE 42

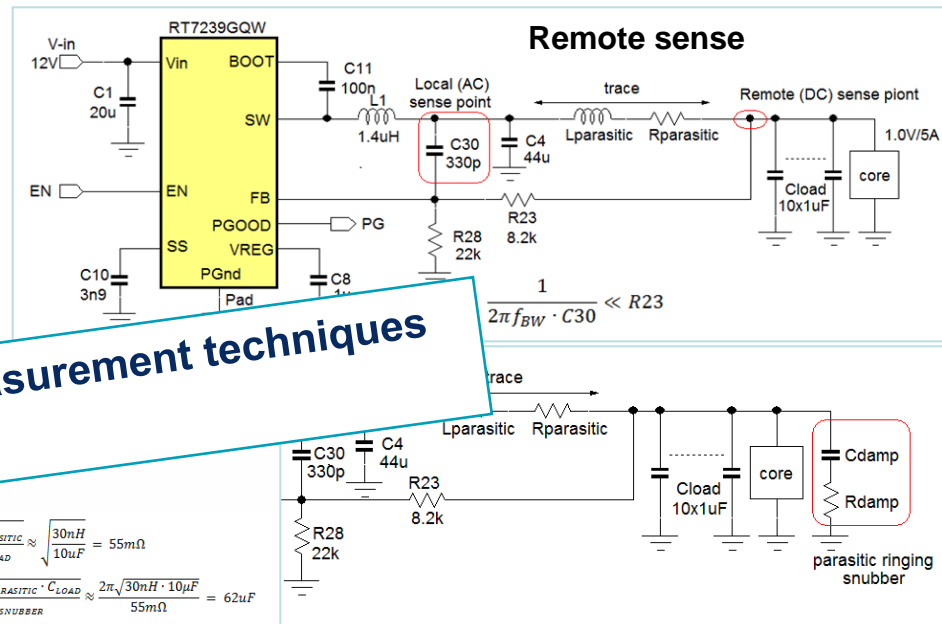

Richtek Designer online tool

Full simulation of application circuit

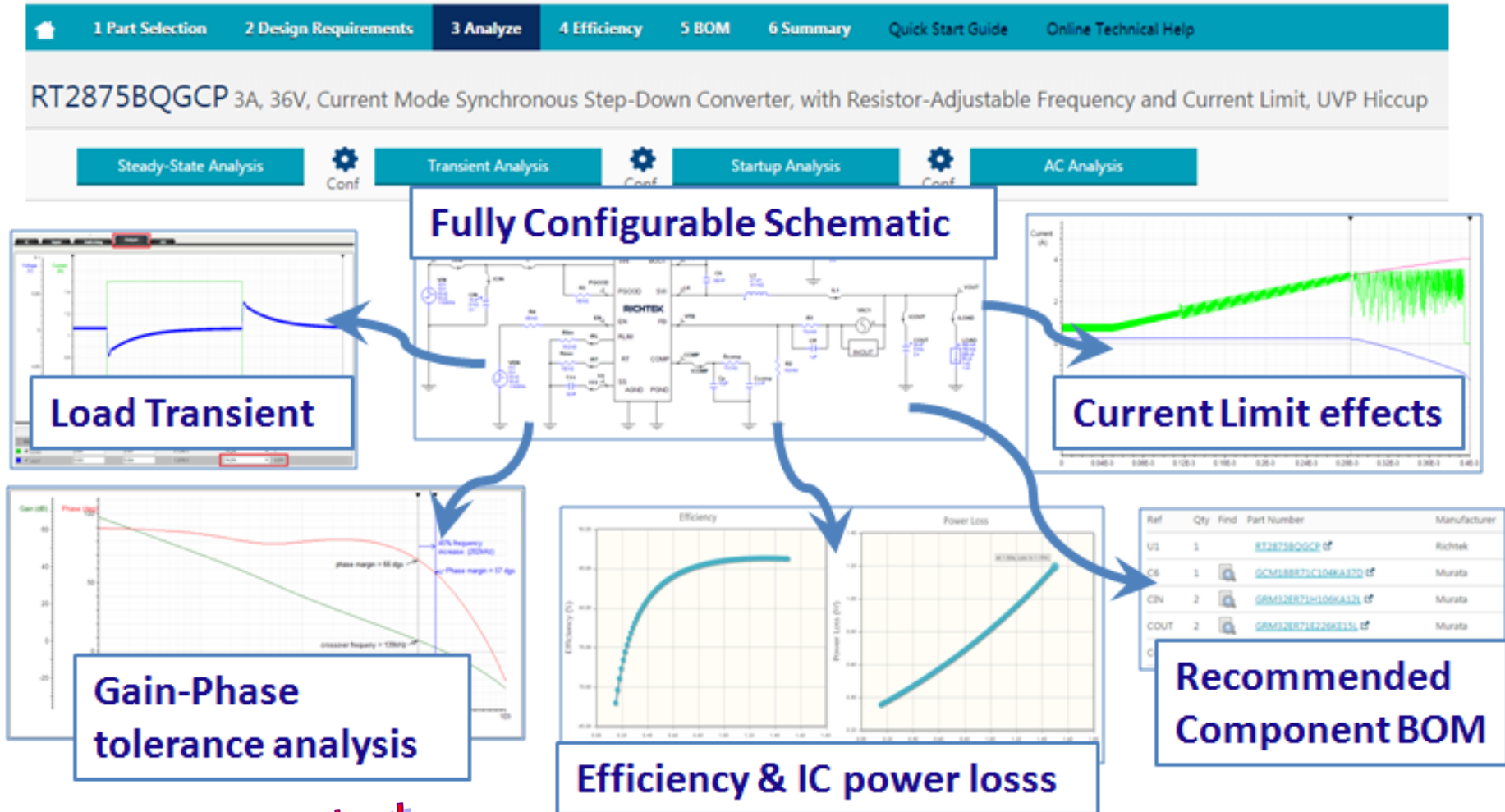

Register today!

RICHTEK
your power partner.

thank you.